

# Circuit Model Components

## Revision

Charge  $q$  coulomb (C)     $e^- = -1.6 \times 10^{-19} C$     proton  $= 1.6 \times 10^{-19} C$


Current  $i \triangleq \frac{dq}{dt}$  amps (A)


 1C positive charge in 1s = 1A

Voltage Potential  $v \triangleq \frac{dw}{dq}$  volts (V) amount of work to make 1C of charge from - to +

  $V_{AB} \triangleq V_A - V_B$      $V_{BA} \triangleq V_B - V_A$      $V_{AB} = -V_{BA}$

Power  $p \triangleq \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = vi$  watt (W)

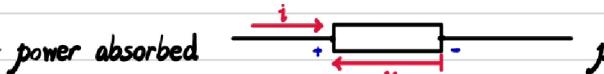power absorbed   $p = vi$

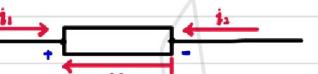power absorbed = - power supplied   $p = vi_1 = -vi_2$

## Independent Ideal Sources

voltage source



current source




## Voltmeter and Ammeters

voltmeter




ammeter

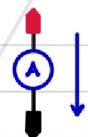


## Circuit

open-circuit

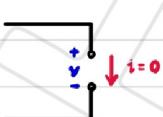

short-circuit

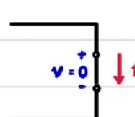

Ohm's Law for linear resistors  $R = \frac{v}{i}$  ohm ( $\Omega$ )

  $v = Ri_1 = -Ri_2$


\* conductance  $G = \frac{1}{R}$  siemens (S)



series resistors  $R_{\text{total}} = \sum R_i$

parallel resistors  $\frac{1}{R_{\text{total}}} = \sum \frac{1}{R_i}$

### Delta-wye transformation \*

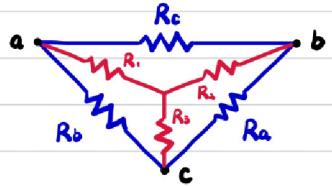

Delta configuration  $R_a = \frac{R_a R_b + R_a R_c + R_b R_c}{R_a}$

Wye configuration  $R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$

### KCL (Kirchhoff's Current Law)


conservation of charge total current in = total current out



$$i_1 + i_2 = i_3 + i_4 + i_5$$
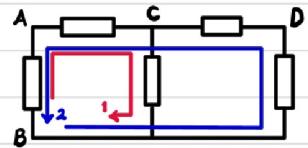
### KVL (Kirchhoff's Voltage Law)

conservation of energy  $\Sigma$  voltage around any closed loop = 0



$$\text{Loop 1} \quad V_{AB} + V_{CA} + V_{BC} = 0$$

$$\text{Loop 2} \quad V_{BD} + V_{DC} + V_{CA} + V_{AB} = 0$$

## Independent and Dependent Sources

### Independent battery

voltage source

$R \rightarrow 0$

current source

$R \rightarrow \infty$

### Dependent amplifier

voltage source

VCVS (Voltage Controlled Voltage Source)  $V_{AB} = kV_{CD}$



CCVS (Current Controlled Voltage Source)  $V_{AB} = k i_2$



current source

YCCS (Voltage Controlled Current Source)  $i_1 = kV_{CD}$




CCCS (Current Controlled Current Source)  $i_1 = k i_2$
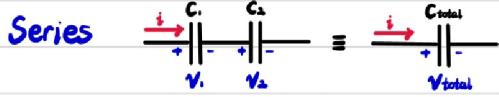
## Capacitors $\text{---} \parallel \text{---}$

Capacitor  $C = \frac{q}{v} \rightarrow i = C \frac{dv}{dt} \rightarrow v = \frac{1}{C} \int i dt$  farad (F)  $\lfloor$  can be discontinuous

steady-state when  $\frac{dv}{dt} = 0 \rightarrow i = 0 \rightarrow$  equivalent to open-circuit



$$V_{\text{total}} = \sum V_i \rightarrow \frac{dV_{\text{total}}}{dt} = \sum \frac{dv_i}{dt} \rightarrow \frac{i}{C_{\text{total}}} = \sum \frac{i}{C_i} \rightarrow \frac{1}{C_{\text{total}}} = \sum \frac{1}{C_i}$$

Parallel  $i_{\text{total}} = \sum i_i \rightarrow \int i_{\text{total}} dt = \sum \int i_i dt \rightarrow V_{C_{\text{total}}} = \sum V_{C_i} \rightarrow C_{\text{total}} = \sum C_i$

## Inductors $\text{---} \sim \sim \sim$

Inductor  $v = L \frac{di}{dt} \rightarrow i = \frac{1}{L} \int v dt$  henry (H)  $\lfloor$  can be discontinuous

steady-state when  $\frac{di}{dt} = 0 \rightarrow v = 0 \rightarrow$  equivalent to short-circuit

Series  $V_{\text{total}} = \sum V_i \rightarrow \int V_{\text{total}} dt = \sum \int V_i dt \rightarrow i L_{\text{total}} = \sum i L_i \rightarrow L_{\text{total}} = \sum L_i$

Parallel  $i_{\text{total}} = \sum i_i \rightarrow \frac{di_{\text{total}}}{dt} = \sum \frac{di_i}{dt} \rightarrow \frac{V}{L_{\text{total}}} = \sum \frac{V}{L_i} \rightarrow \frac{1}{L_{\text{total}}} = \sum \frac{1}{L_i}$

## DC Circuit Analysis

### Nodal Analysis

Recipe ① mark reference node / ground and label nodes

② apply KCL at each node and label currents through branches / omit earth


③ write currents as function of node voltages

④ plug in knowns and solve for unknowns linear algebra

no connection  or 

connection 

Example

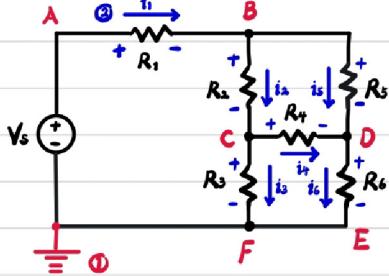

① show in diagram above

② At B,  $i_1 = i_2 + i_5$ ; At C,  $i_3 = i_4 + i_7$ ; At D,  $i_4 + i_5 = i_6$

$$③ \text{At } B, \frac{V_{AB}}{R_1} = \frac{V_{AC}}{R_2} + \frac{V_{BD}}{R_5}; \text{At } C, \frac{V_{BC}}{R_2} = \frac{V_{CF}}{R_3} + \frac{V_{CD}}{R_4}; \text{At } D, \frac{V_{CD}}{R_4} + \frac{V_{BD}}{R_5} = \frac{V_{DE}}{R_6}$$


$$\therefore \frac{V_A - V_B}{R_1} = \frac{V_B - V_C}{R_2} + \frac{V_B - V_D}{R_5}; \frac{V_B - V_C}{R_2} = \frac{V_C - V_F}{R_3} + \frac{V_C - V_D}{R_4}; \frac{V_C - V_D}{R_4} = \frac{V_D - V_E}{R_5} + \frac{V_D - V_E}{R_6}$$

$$\therefore V_A = V_s = V_A - V_E \quad \therefore V_E = 0V$$

④ .....


## Equivalent Circuits

Thevenin equilibrium circuit

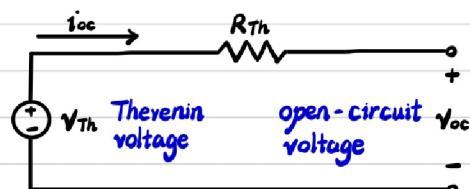

open-circuit  $\rightarrow i_{oc} = 0$

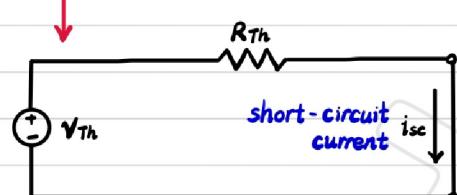
$$\text{KVL} \rightarrow V_{th} - i_{oc} R_{th} = V_{oc} \rightarrow V_{th} = V_{oc}$$



short-circuit  $\rightarrow i_{sc} = \frac{V_{th}}{R_{th}}$


$$\rightarrow R_{th} = \frac{V_{th}}{i_{sc}}$$

Norton equivalent circuit

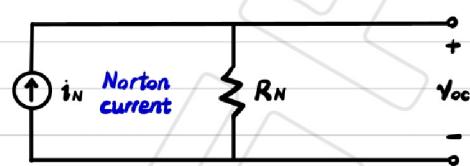

open-circuit
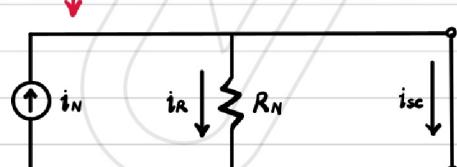
$$\text{KVL} \rightarrow V_{oc} = i_N R_n \rightarrow R_n = \frac{V_{oc}}{i_N}$$



short-circuit  $\rightarrow V_{sc} = 0 \rightarrow i_R = \frac{V_{sc}}{R_n} = 0$



$$\text{KCL} \rightarrow i_N = i_R + i_{sc} \rightarrow i_N = i_{sc} \rightarrow R_n = R_{th}$$

**Recipe** ① compute / measure  $V_{oc} = V_{Th}$  in open-circuit

② compute / measure  $i_{sc} = i_N$  in short-circuit

③ find  $R_{Th} = R_N = \frac{V_{oc}}{i_{sc}}$

**Example**

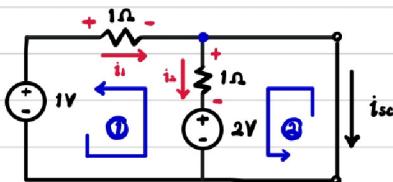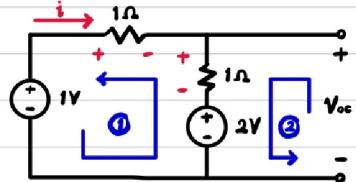

$$\textcircled{1} \text{ find } V_{oc} \text{ KVL } \xrightarrow{\textcircled{1}} 1 - 1 \cdot i - 1 \cdot i - 2 = 0 \text{ (V)} \rightarrow i = -\frac{1}{2} \text{ (A)}$$

$$\xrightarrow{\textcircled{2}} 1 \cdot i + 2 - V_{oc} = 0 \text{ (V)} \rightarrow V_{oc} = 1.5 \text{ (V)} = V_{Th}$$

$$\textcircled{2} \text{ find } i_{sc} \text{ KCL } \rightarrow i_1 = i_2 + i_{sc} \rightarrow i_{sc} = 3 \text{ (A)}$$

$$\text{KVL } \xrightarrow{\textcircled{1}} 1 - 1 \cdot i_1 - 1 \cdot i_2 - 2 = 0 \text{ (V)} \rightarrow i_1 = 1 \text{ (A)}$$

$$\xrightarrow{\textcircled{2}} 1 \cdot i_2 + 2 = 0 \rightarrow i_2 = -2 \text{ (A)}$$

$$\textcircled{3} \text{ find } R_{Th} \quad R_{Th} = R_N = \frac{V_{oc}}{i_{sc}} = 0.5 \text{ (Ω)}$$

for Thevenin equivalent circuit




for Norton equivalent circuit



## Maximum Power Transfer

**Voltage divider rule**

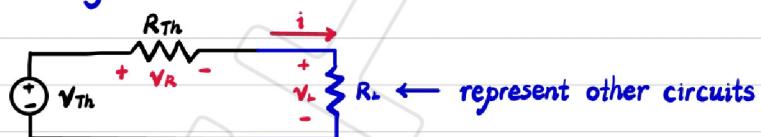

$$\text{Power absorbed by load } P_L = V_L \cdot i$$

$$\text{KVL} \rightarrow V_{Th} - V_R - V_L = 0 \rightarrow V_{Th} - iR_{Th} - iR_L = 0 \rightarrow i = \frac{V_{Th}}{R_{Th} + R_L}$$

$$\rightarrow V_{Th} - iR_{Th} - V_L = 0 \rightarrow V_L = V_{Th} - iR_{Th} = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

$$\rightarrow P_L = \frac{R_L}{(R_{Th} + R_L)^2} (V_{Th})^2$$

Maximised  $P_L$

$$\frac{dP_L}{dR_L} = 0 \rightarrow \frac{(V_{Th})^2 (R_{Th} + R_L)^2 - R_L (V_{Th})^2 \cdot 2 \cdot (R_{Th} + R_L)}{(R_{Th} + R_L)^4} = \frac{(V_{Th})^2 (R_{Th} - R_L)}{(R_{Th} + R_L)^3} = 0 \rightarrow R_{Th} = R_L$$


## Reactive Circuit Transient Response

### Reactive Circuit Transient Response


Aim interested in computing the time response of **RLC circuits** to time-varying sources

Time-varying sources

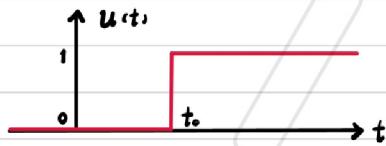unit step  $u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t \geq t_0 \end{cases}$



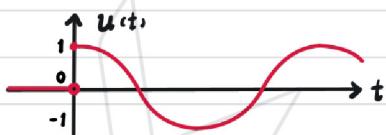Heaviside function  $u(t) \cos(\omega t)$



**Recipe** ① identify the instances  $t_1, t_2, t_3, \dots$  where discrete changes / switches

capacitors  $v_c(t_i^-) = v_c(t_i^+)$  for  $\forall i$

inductors  $i_L(t_i^-) = i_L(t_i^+)$  for  $\forall i$

② if initial condition is not given, assume **steady state** at  $t = t_1^-$

capacitors  $\frac{dv}{dt}(t_1^-) = 0$       inductors  $\frac{di}{dt}(t_1^-) = 0$

sketch circuit for  $t < t_1$ .

replace capacitors as open-circuit  $\text{---} \text{---}$   $\rightarrow$  compute  $v_c(t_i^-)$

replace inductors as short-circuit  $\text{---} \text{---}$   $\rightarrow$  compute  $i_L(t_i^-)$


③ sketch circuit for all intervals,  $t_1 < t < t_2, t_2 < t < t_3, \dots$

④ derive differential equations for circuits in each interval

$$N_{\text{differential equations}} = N_C + N_L = N_{\text{initial conditions}}$$

## ⑤ solve differential equations

Example

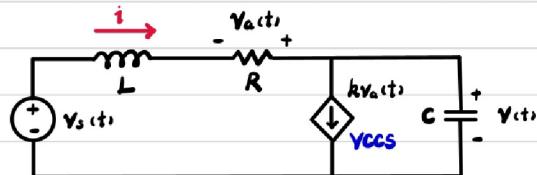


Suppose  $V_s = 6u(t) + 10(V)$ ,  $k = 2$ ,  $L = 0.1(H)$ ,

$R = 4(\Omega)$ ,  $C = 0.625(F)$ , find  $v(t)$

$$\textcircled{1} \quad v(0^-) = v(0^+) \text{ and } i(0^-) = i(0^+)$$


\textcircled{2} for  $t < 0$ .

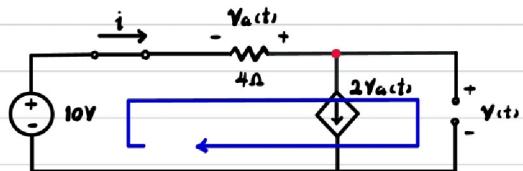

$$KCL \rightarrow i(0^-) = kV_a(0^-) = 2 \cdot [4 - i(0^-)] \rightarrow i(0^-) = 0(A) \rightarrow V_a(0^-) = 0(V)$$

$$KVL \rightarrow 10 + V_a(0^-) - V(0^-) = 0(V) \rightarrow V(0^-) = 10(V)$$

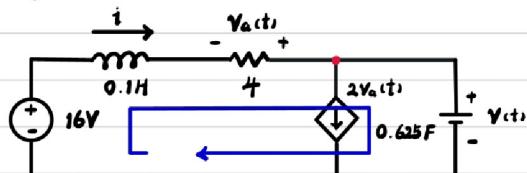for  $t > 0$ ,  $i(0^+) = i(0^-) = 0(A)$  and  $v(0^+) = V(0^-) = 10(V)$



$$KCL \rightarrow i(t) = kV_a(t) + C \frac{dv}{dt} = kR[-i(t)] + C \frac{dv}{dt} \rightarrow \frac{dv}{dt} = \frac{1+kR}{C} i(t) = \frac{72}{5} i(t) \leftarrow$$

$$KVL \rightarrow 16 - L \frac{di}{dt} + V_a(t) - V(t) = 0 \rightarrow 16 - L \frac{di}{dt} + R[-i(t)] - V(t) = 0$$

$$\rightarrow 16 - 0.1 \frac{di}{dt} - 4i - V = 0 \leftarrow$$

$$\rightarrow \frac{di}{dt} + 40i + 10V = 160 \rightarrow \frac{5}{72} \frac{dv}{dt} + \frac{25}{9} \frac{dv}{dt} + 10V = 160$$

$$\rightarrow \frac{dv}{dt} + 40 \frac{dv}{dt} + 144V = 2304$$

$$\rightarrow V(t) = 0.75e^{-4t} - 6.75e^{-36t} + 16(V) \text{ for } t > 0$$

## Operational Amplifier


Operation Amplifier (Op-amp)

Circuit diagram




## Feedback configuration

negative feedback

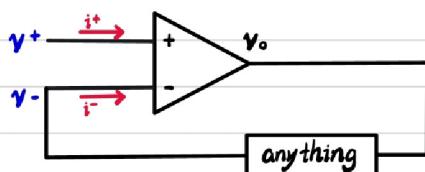

positive feedback

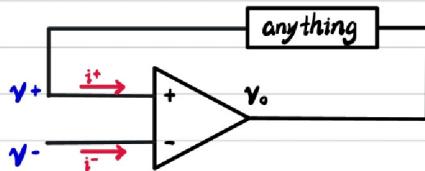


$$\begin{aligned} \cdot V_- < V_+ &\rightarrow V_o \uparrow \\ \cdot V_+ > V_- &\rightarrow V_o \downarrow \end{aligned}$$

balanced quickly


①  $i^- = i^+ \xrightarrow{\text{infinity } R} 0A$

②  $V_- = V_+$

## Voltage follower / buffer

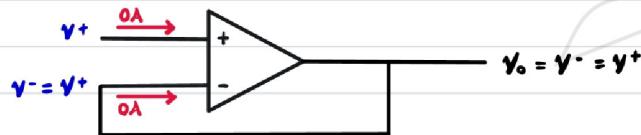


## example

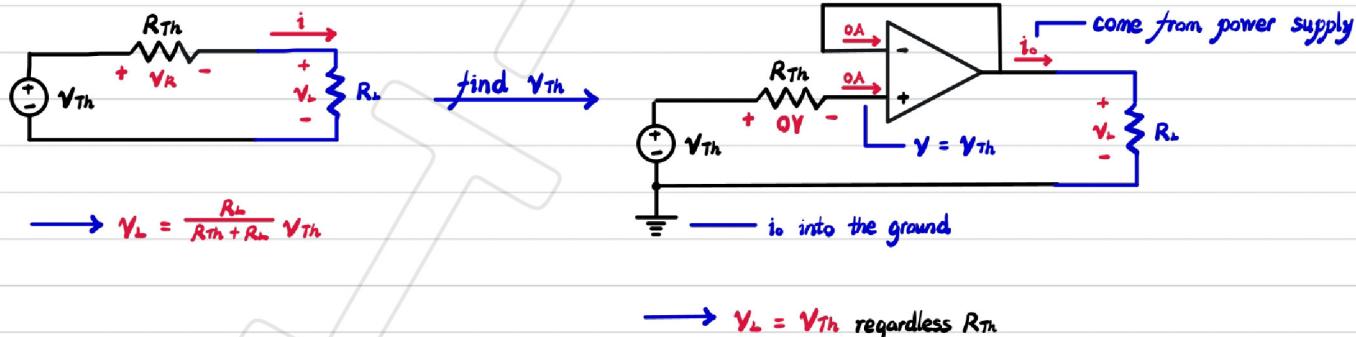

## Non-inverting amplifier



## Inverting summing amplifier

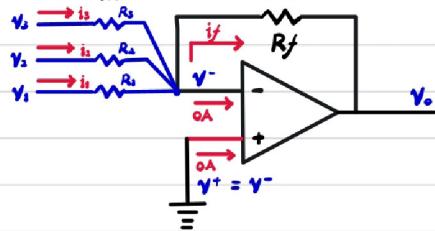

$$KCL \rightarrow i_f + 0A = i_1 + i_2 + i_3$$


$$\rightarrow \frac{V^- - V_o}{R_f} = \frac{V_1 - V^-}{R_1} + \frac{V_2 - V^-}{R_2} + \frac{V_3 - V^-}{R_3}$$

$$\rightarrow -\frac{V_o}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$* V^+ = V^- = 0V$$

$$\rightarrow V_o = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

## Inverting amplifier

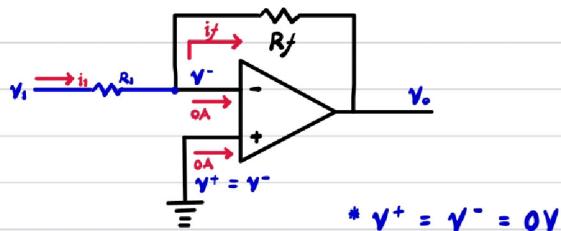


$$V_o = -\frac{R_f}{R_1} V_1$$


> 1  
amplify

< 1  
attenuates 减弱

in series → non-inverting amplifier

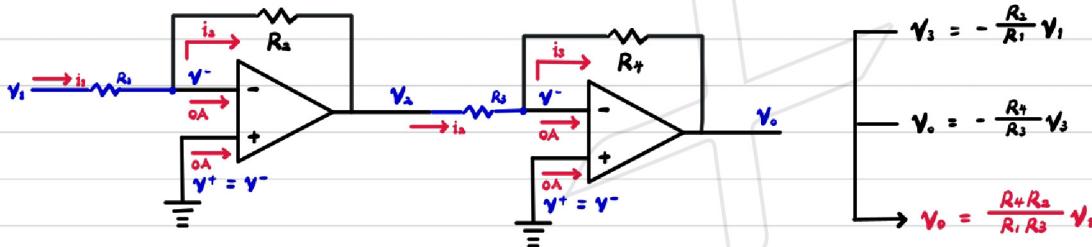

## Inverting integrator

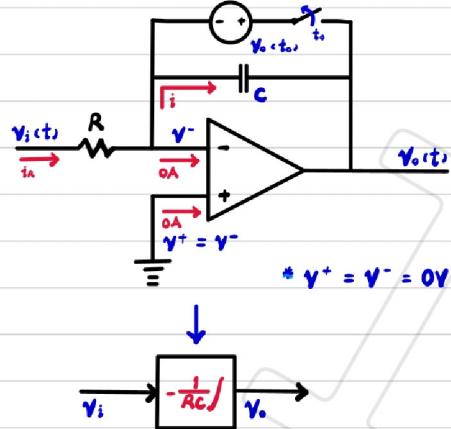

$$KCL \rightarrow i_R = i + 0A$$

$$t \geq t_0 \rightarrow i_R = \frac{V_i - V^-}{R} = \frac{V_i}{R} = i = C \frac{d}{dt} [V^- - V_o(t)] = -C \frac{dV_o}{dt}$$

$$\rightarrow \frac{dV_o}{dt} = -\frac{1}{RC} V_i(t)$$

$$\rightarrow V_o(t) - V_o(t_0) = -\frac{1}{RC} \int_{t_0}^t V_i(\tau) d\tau$$

$$\rightarrow V_o(t) = V_o(t_0) - \frac{1}{RC} \int_{t_0}^t V_i(\tau) d\tau$$

## Differential and Algebraic Equations

Design and solution of differential and algebraic equations

example


implement a circuit that solves the equation

$$\ddot{q}(t) + k\dot{q}(t) + lq(t) = ax(t) + by(t), \quad q(0) = q_0, \quad \dot{q}(0) = r_0$$


where  $x$  and  $y$  are the inputs and  $q$  is output of the circuit

①  $\ddot{q}(t) = ax(t) + by(t) - k\dot{q}(t) - lq(t)$

② draw a block diagram

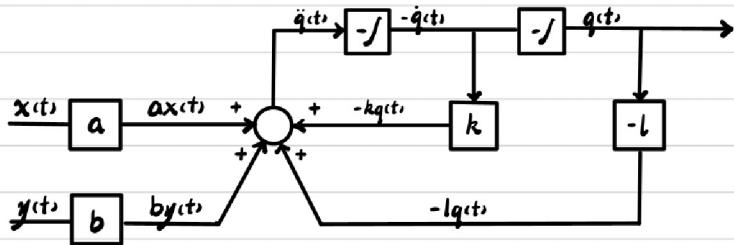

③ substitute Op-amp choose  $RC = 1$

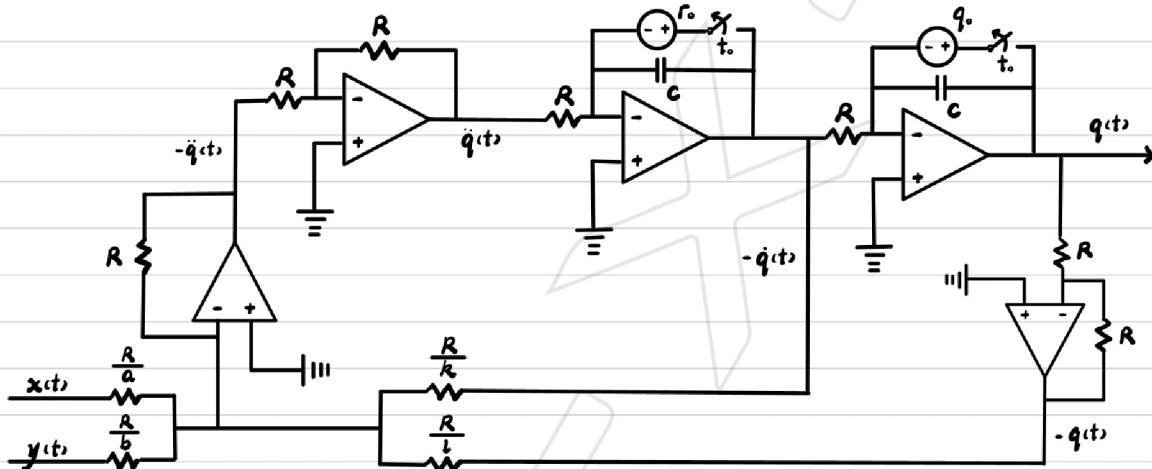

\* typical range       $R \quad 100\Omega \sim 100k\Omega$        $C \quad 1\mu F \sim 100mF$

$i \quad 1\mu A \sim 1mA$        $v \quad 1mV \sim 10mV$

\* why not differentiators?

example

measure  $x(t) = s(t) + n(t) = s(t) + \sum_n a_n \sin(\omega_n t)$

signal      noise      not interested in

$$\rightarrow \frac{dx}{dt} = \frac{ds}{dt} + \sum_n a_n \omega_n \cos(\omega_n t)$$

$\downarrow > 1 \rightarrow \text{amplify noise}$

# DC Motors and Generators \*

## DC Motors

### Linear Motors

horizontal (Lorentz) force

$$\vec{f} = I\vec{L} \times \vec{B}$$


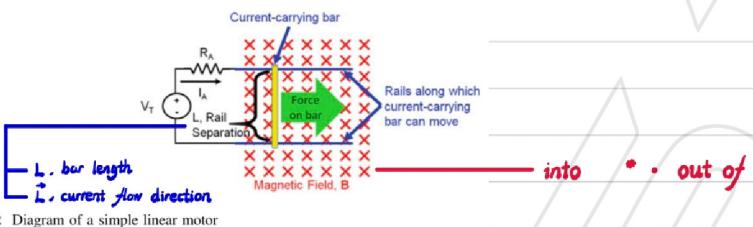
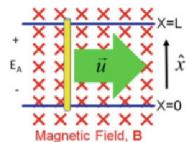


Fig. 5.3 Right-hand rule to find the direction of force for linear motor


In this case

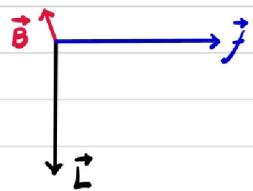

conductor cuts across  $\vec{B}$   $\rightarrow$  voltage induced

$$E_A = uLB$$

Fig. 5.5 Electromotive force (emf) induced due to motion of conducting bar in the presence of a magnetic field

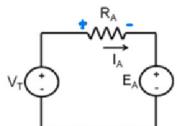

KVL  $\sum V = 0$  in close loop  $V_T - R_A I_A - E_A = 0$

$$\rightarrow I_A = \frac{V_T - E_A}{R_A} = \frac{V_T - uLB}{R_A} \propto -u \text{ also } f \propto I_A$$

Fig. 5.6 Equivalent circuit for a linear machine

$\rightarrow$  balance to have constant  $u$

### Rotating DC Motors

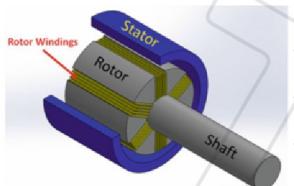


Fig. 5.8 Basic structure of DC motor

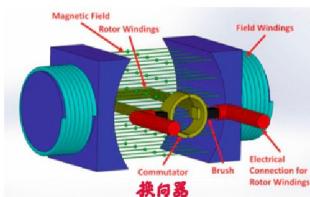


Fig. 5.9 Simplified diagram for DC motor focusing on a single rotor winding to illustrate the motor operation


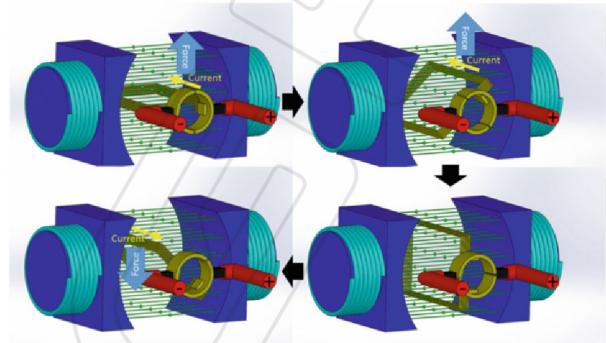


Fig. 5.10 Diagram illustrating basic motor operation emphasizing the importance of the commutator to change current direction so that the Lorentz force, and hence the torque, can always be in the same direction as the motor turns

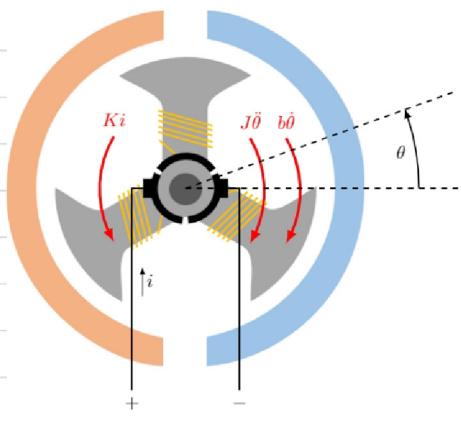

$$J\ddot{\theta} = T_{out} = T_{der} - T_{loss}$$

\* different source of losses

- $T_{fluid} \propto \omega^2 = \dot{\theta}^2$  — ignore unless very high speed

- $T_{viscous} \propto \omega = \dot{\theta}$  — dominate

$$\rightarrow T_{loss} = b\dot{\theta} \rightarrow J\ddot{\theta} = T_{der} - b\dot{\theta}$$

Torque on the rotor (due to Lorentz force)

$$T_{der} = K\phi I_A = \tilde{K}_t I_A$$

constant torque constant  
magnetic flux produced by each stator pole 定子极

$$\text{Back emf } E_A = \tilde{K}_a \omega = \tilde{K}_a \dot{\theta}$$

$$\text{Power generated } P_{der} = T_{der} \omega = \tilde{K}_t I_A \omega = \text{absorbed } P_A = E_A I_A = \tilde{K}_a \omega I_A \rightarrow K = \tilde{K}_t = \tilde{K}_a$$


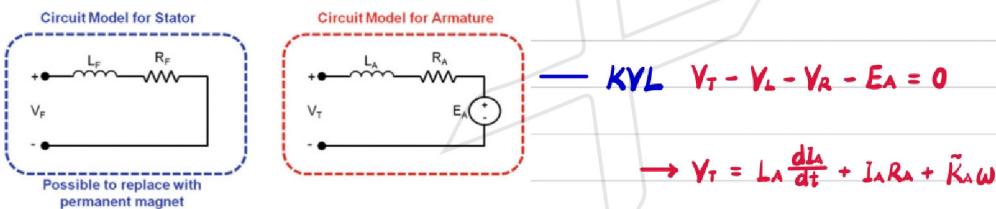


Fig. 5.11 Circuit model for DC motor

$$\rightarrow \begin{cases} V_T = L_A \dot{I}_A + R_A I_A + K \dot{\theta} \\ J\ddot{\theta} = K I_A - b\dot{\theta} \end{cases} \rightarrow \begin{bmatrix} \dot{I}_A \\ \dot{\theta} \end{bmatrix} = \begin{bmatrix} \frac{1}{L_A} (V_T - R_A I_A - K \dot{\theta}) \\ \frac{1}{J} (K I_A - b\dot{\theta}) \end{bmatrix}$$

PWM (Pulse Width Modulation)

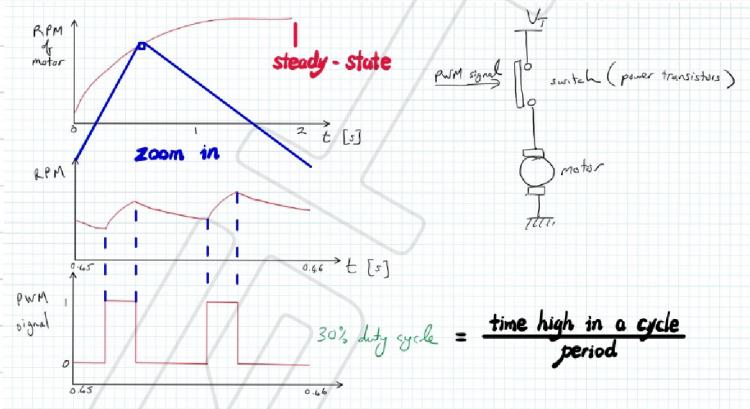


period logical signal

switching between 0 to 1



A/D (Analogue 模拟的 to digital) and D/A Conversion

# Microprocessor Control System

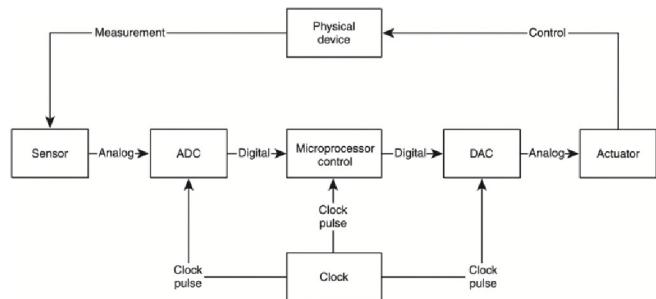

## DAC (Digital-to-Analogue Conversion)

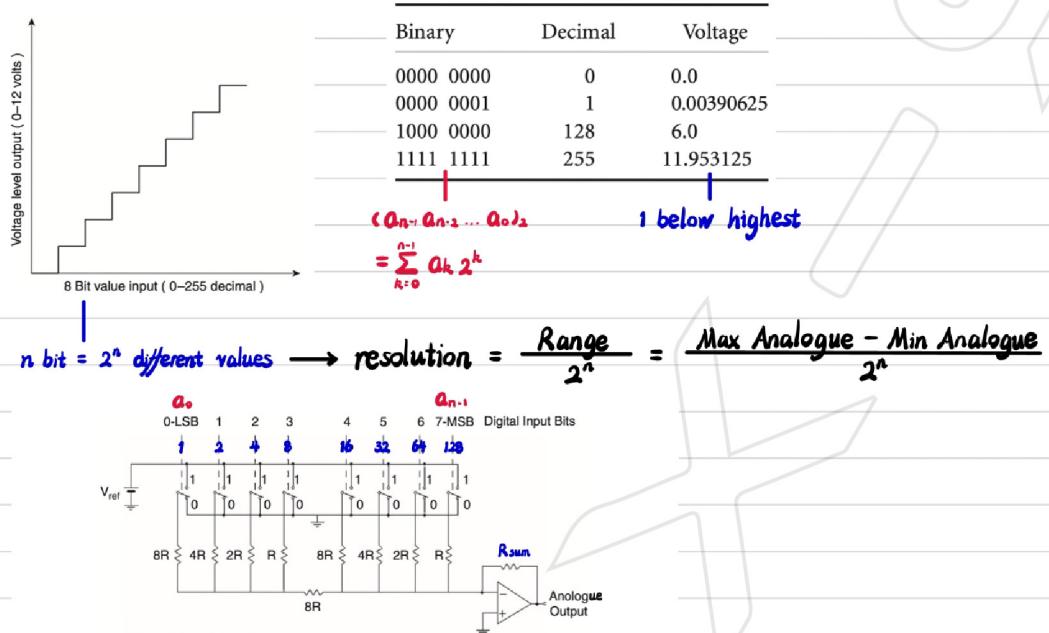


FIGURE 31.5 DAC architecture—most digital-to-analog converters (DAGs) follow a standard architecture of a switch network, a resistive network, and an amplifier.

## ADC (Analogue-to-Digital Conversion)

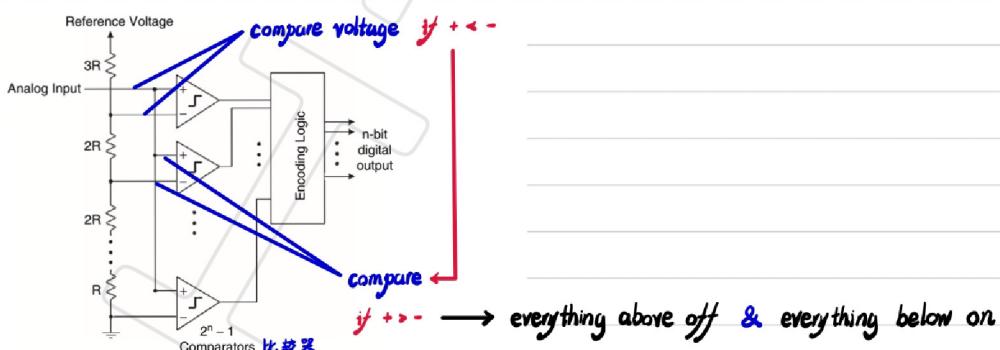


FIGURE 31.1 Flash ADC—a flash converter has  $2^n - 1$  comparators operating in parallel. It relies on the uniformity of the resistors for linearity.

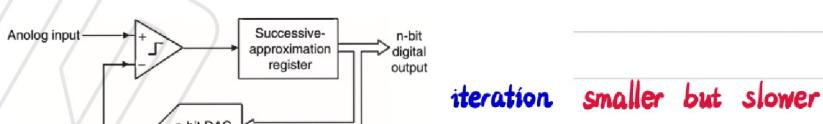


FIGURE 31.2 SAR ADC—a successive-approximation (SAR) converter has one comparator that iterates through a series of “guesses” to determine a digital representation of the signal.

## Nyquist Sampling Theorem

sample **twice** as fast as highest frequency component to reconstruct signal

