
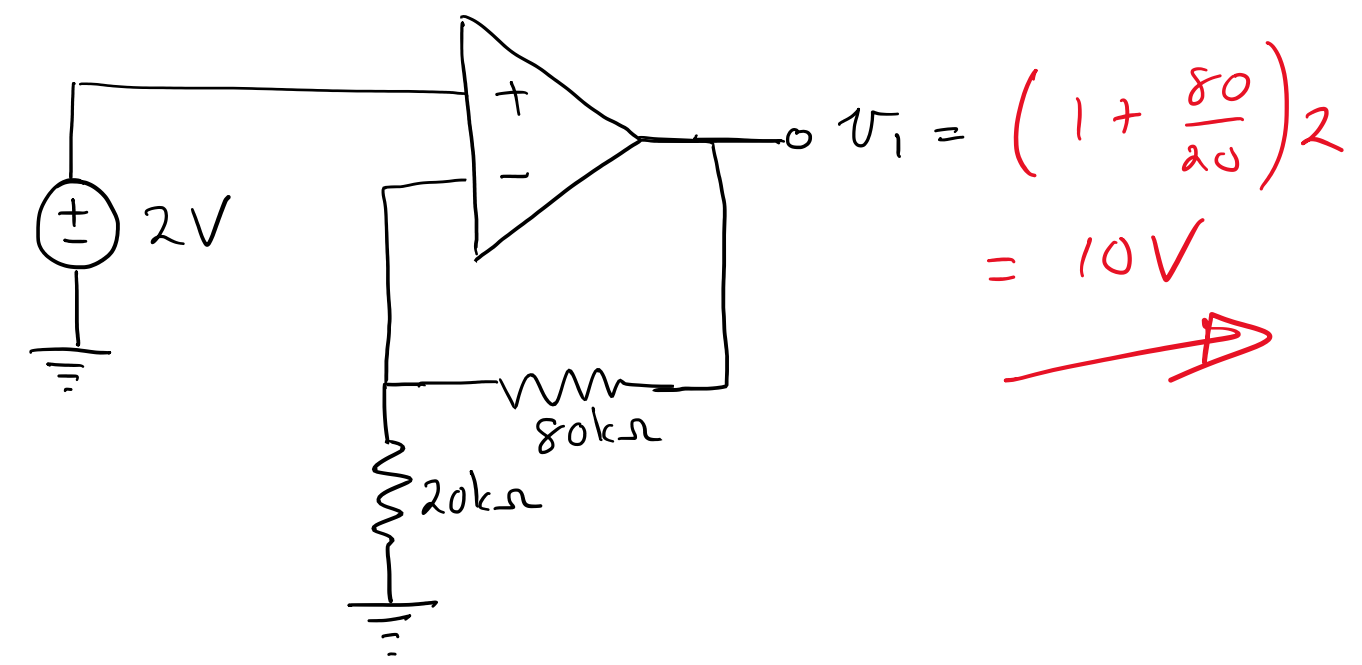



Q1

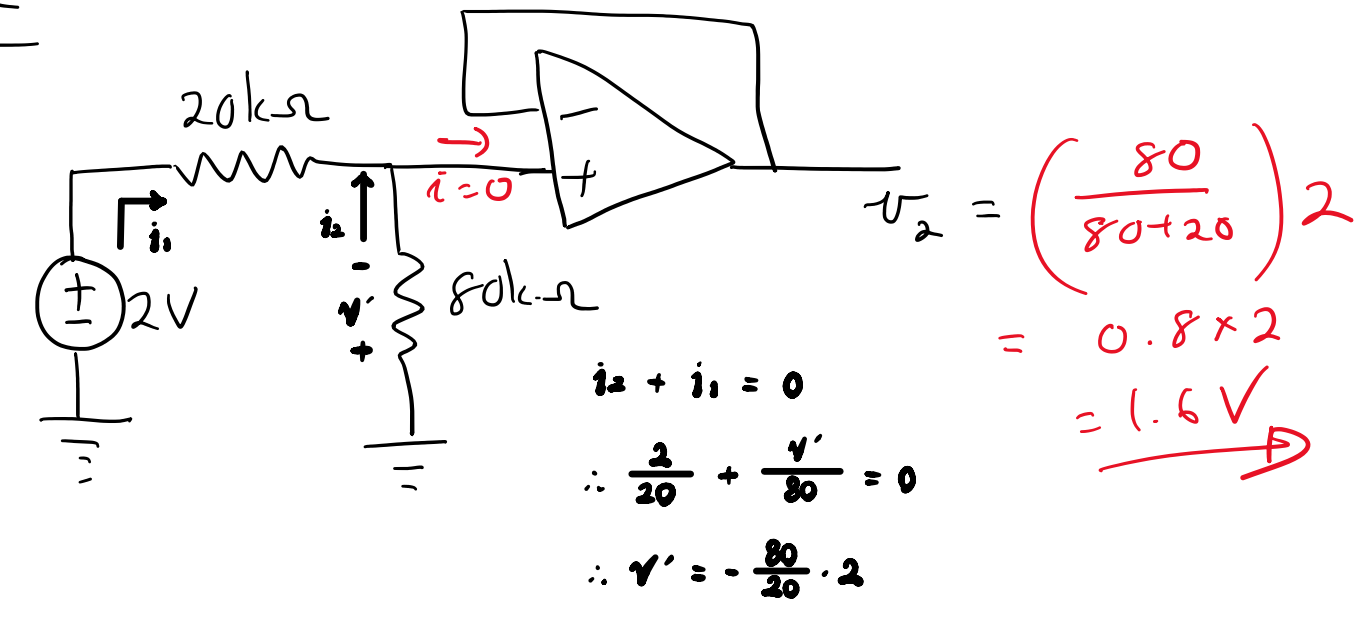


Q2




Q3

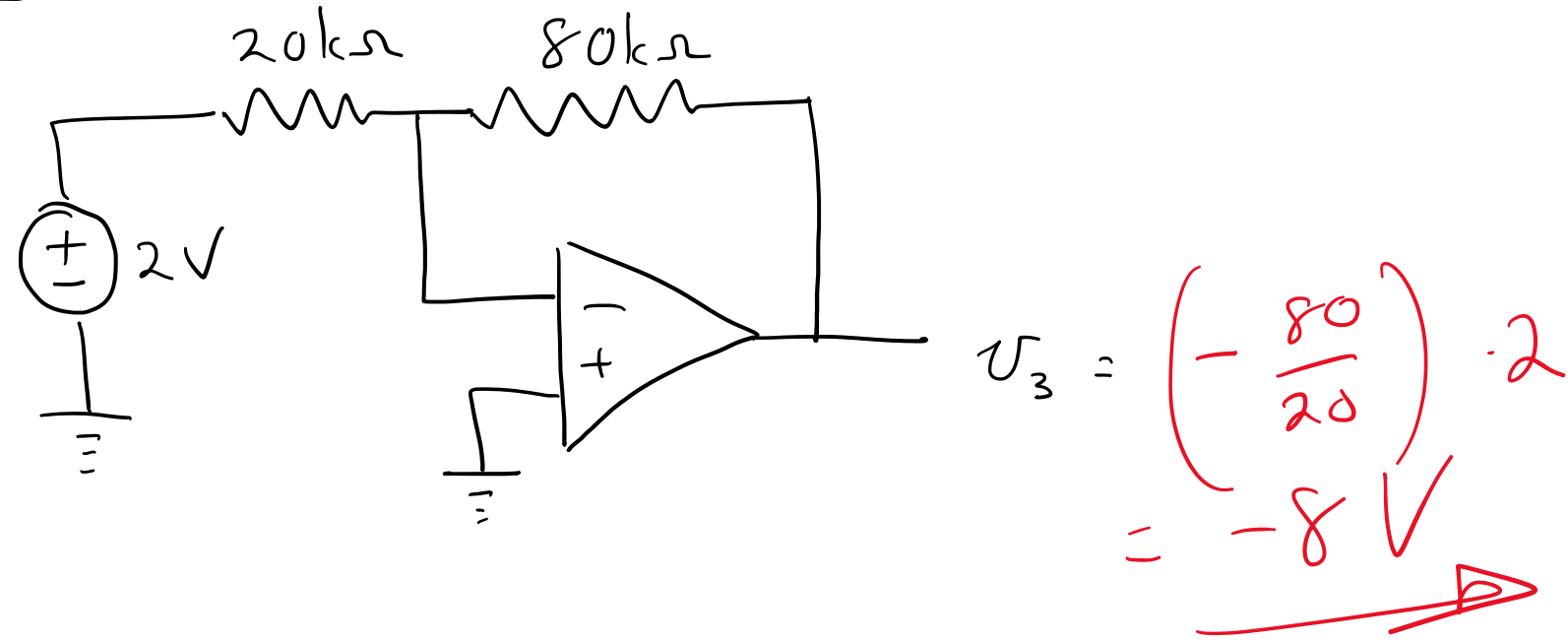


Q4

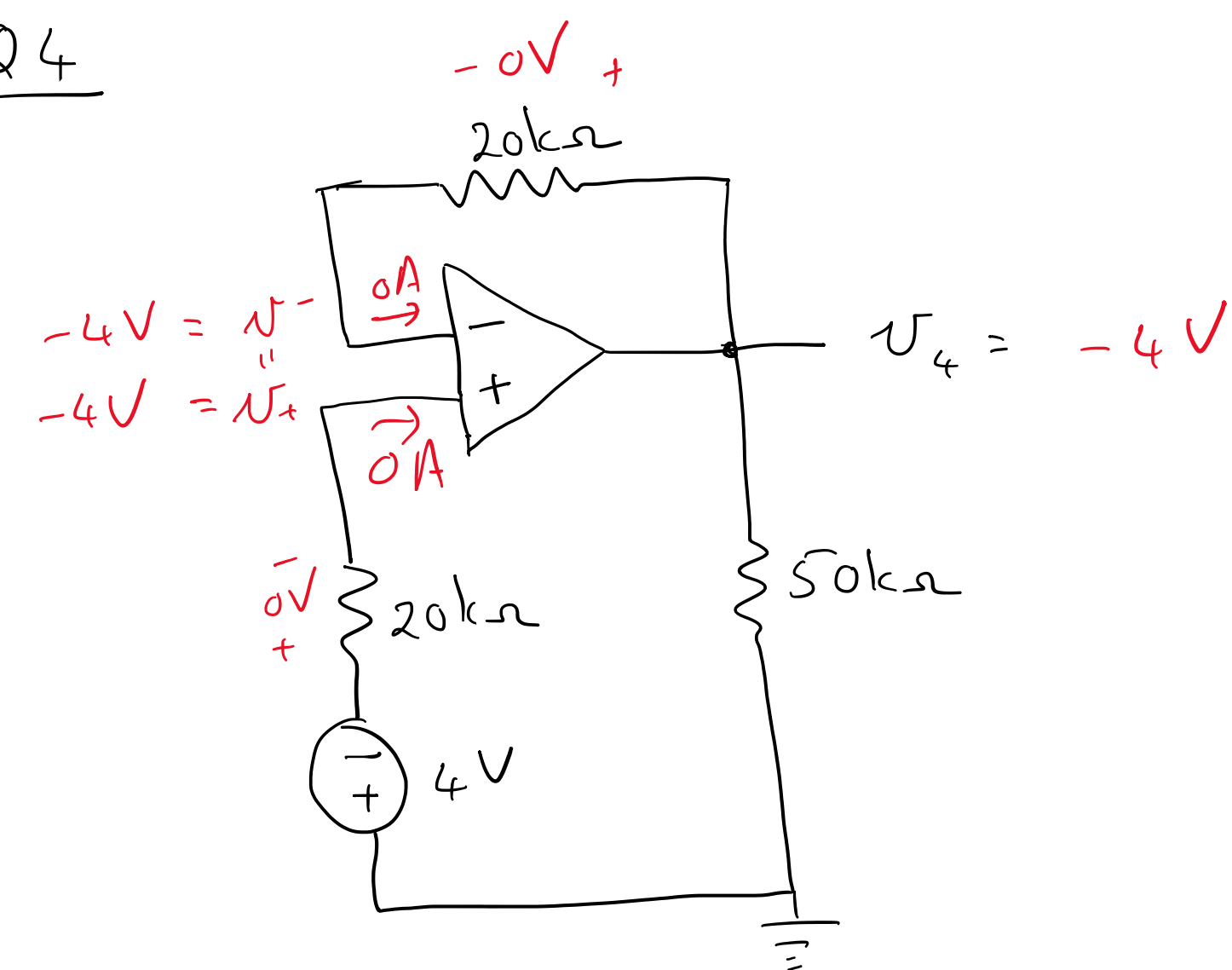


Q5

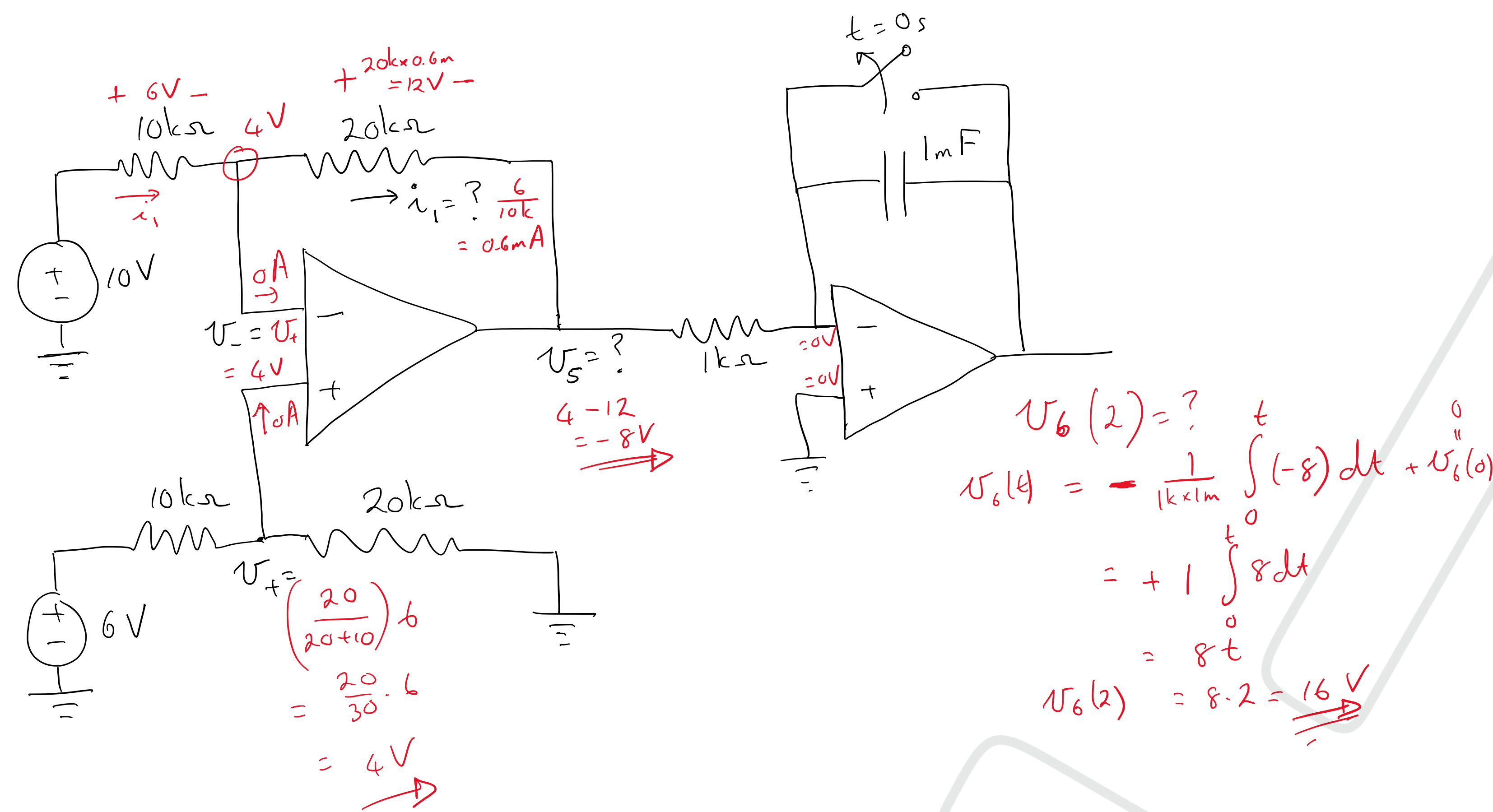


Non-inverting amplifier

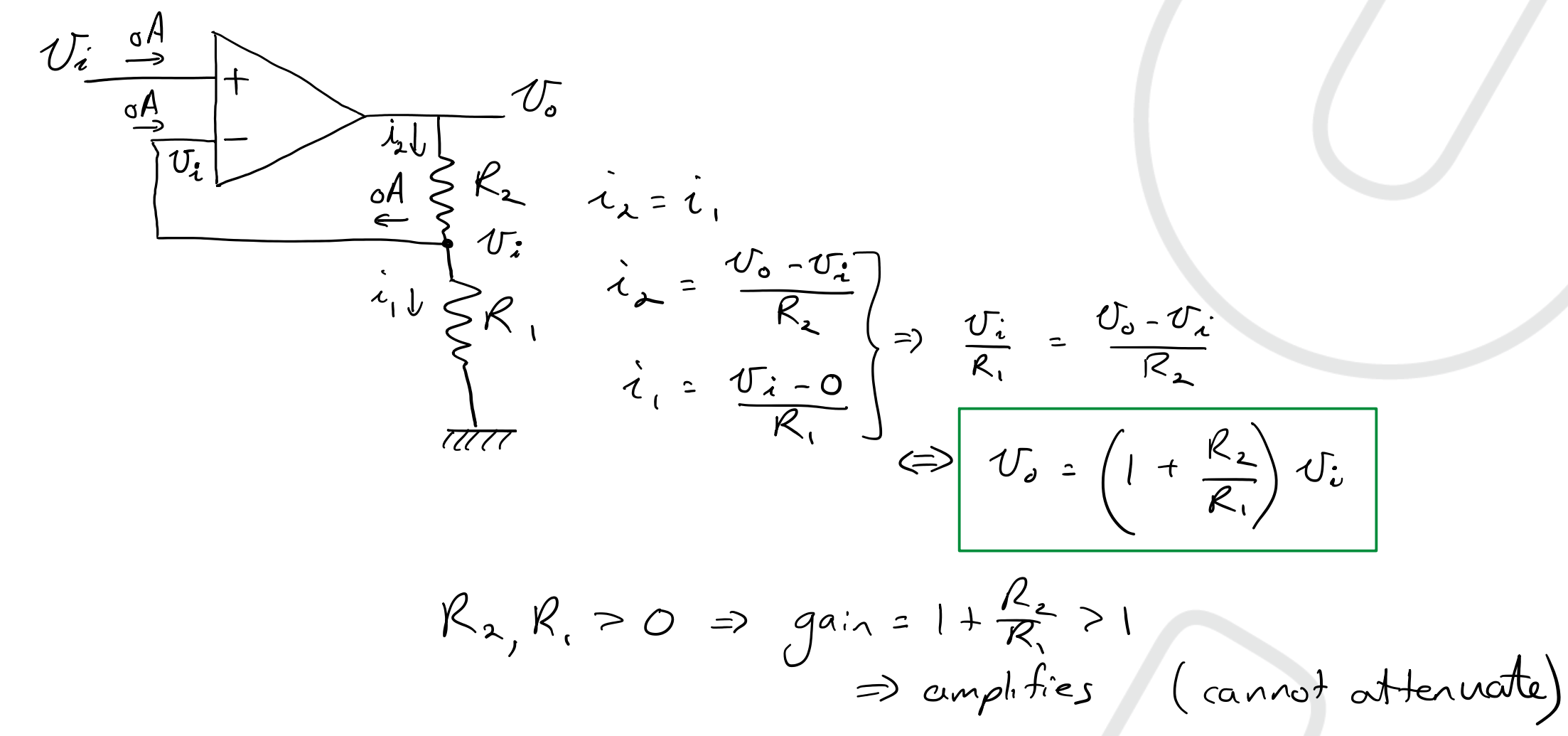


Inverting summing amplifier

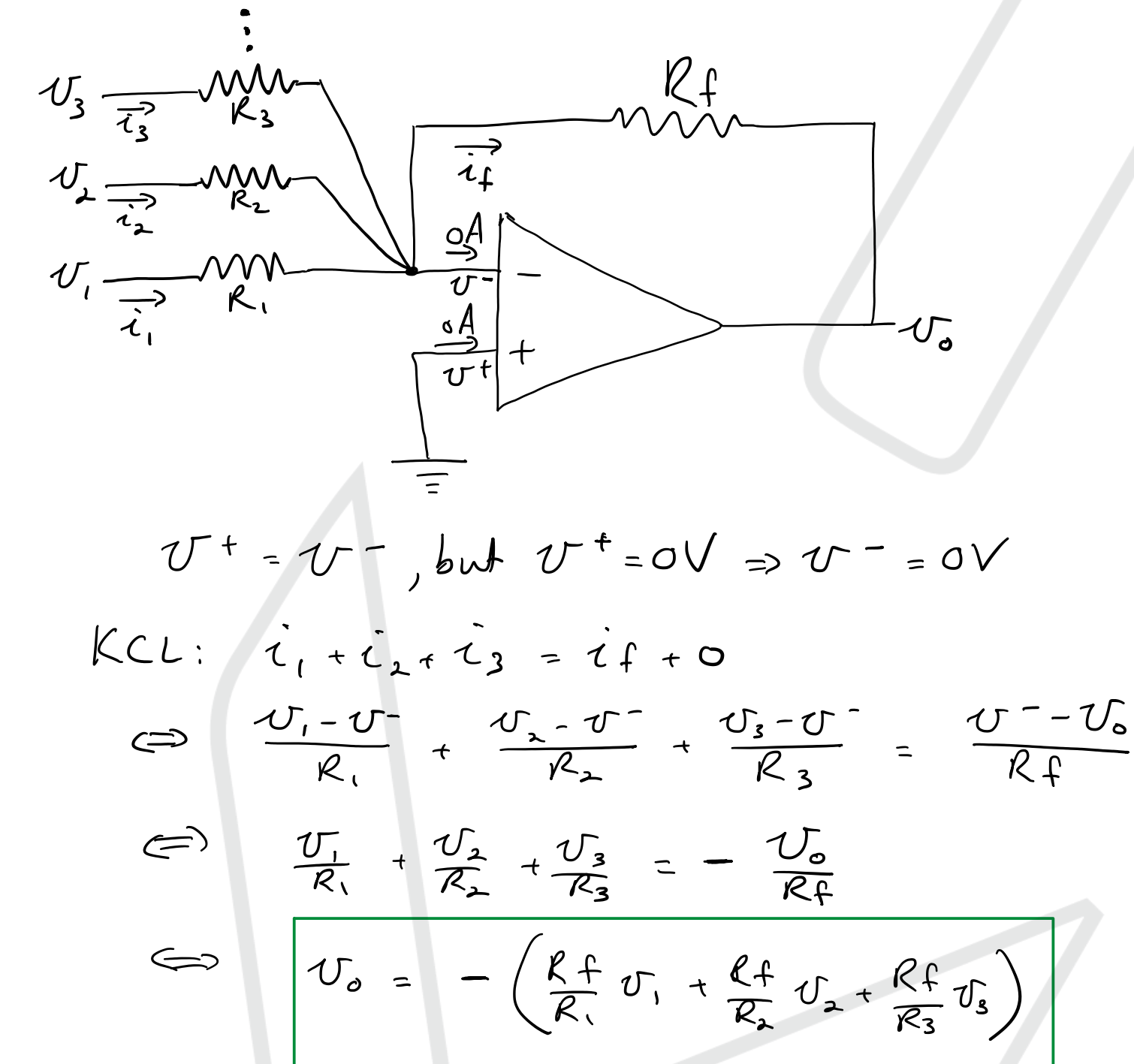

Inverting amplifier

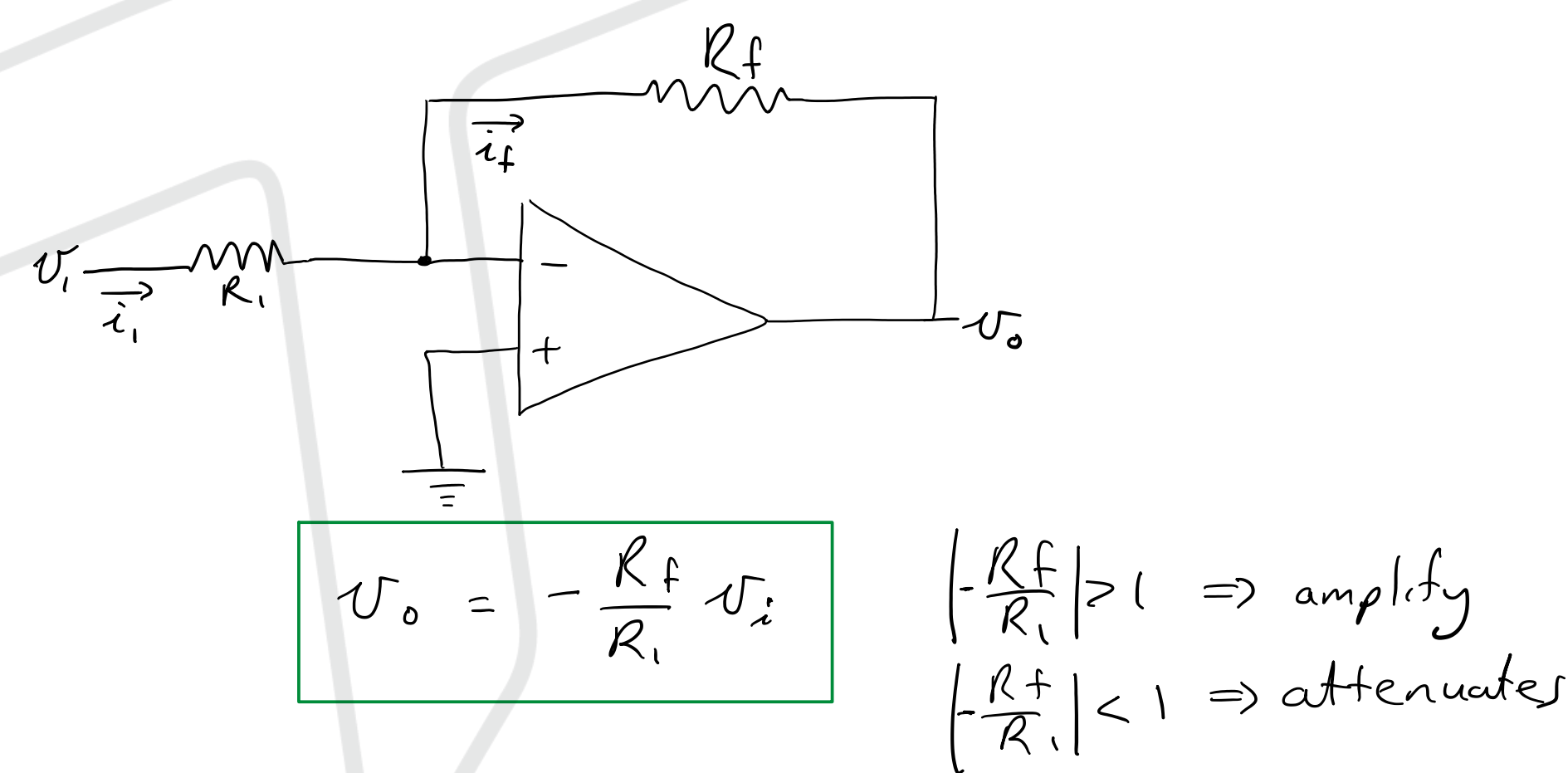

Non-inverting amplifier

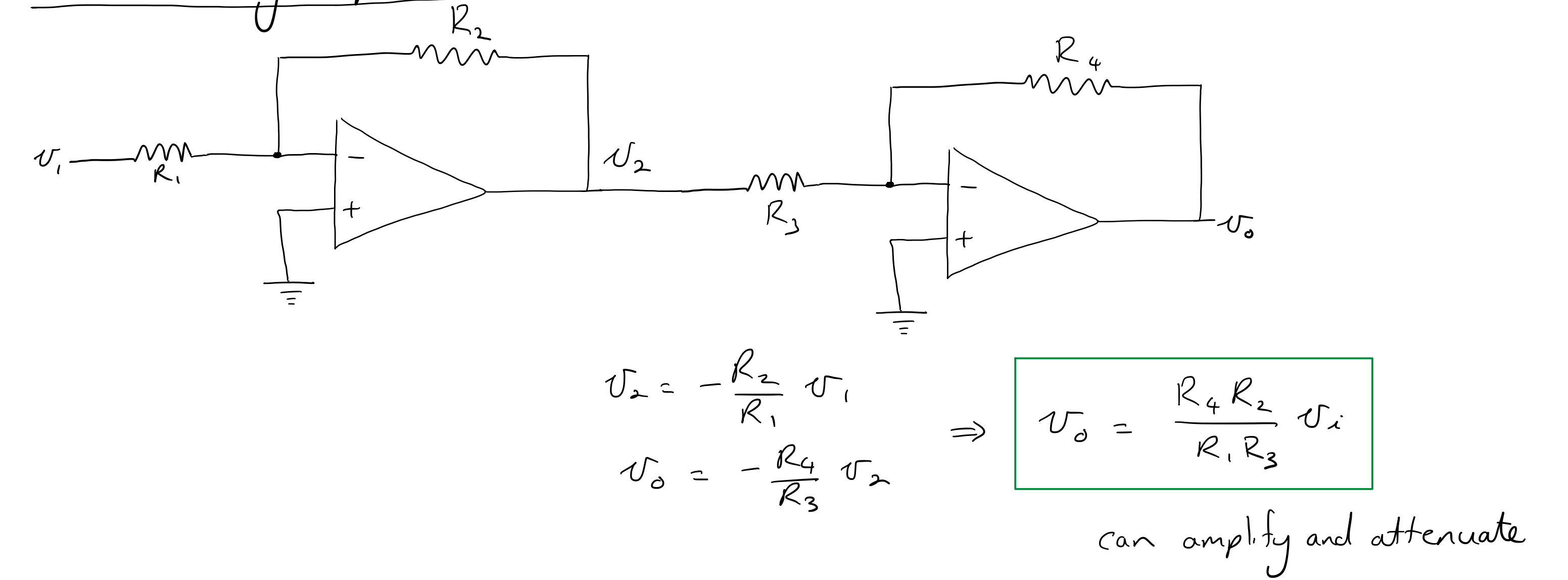

Inverting integrator

